




# ECE 554: Minilab 1



Simulation & debugging



# Minilab 0 - Minilab 1

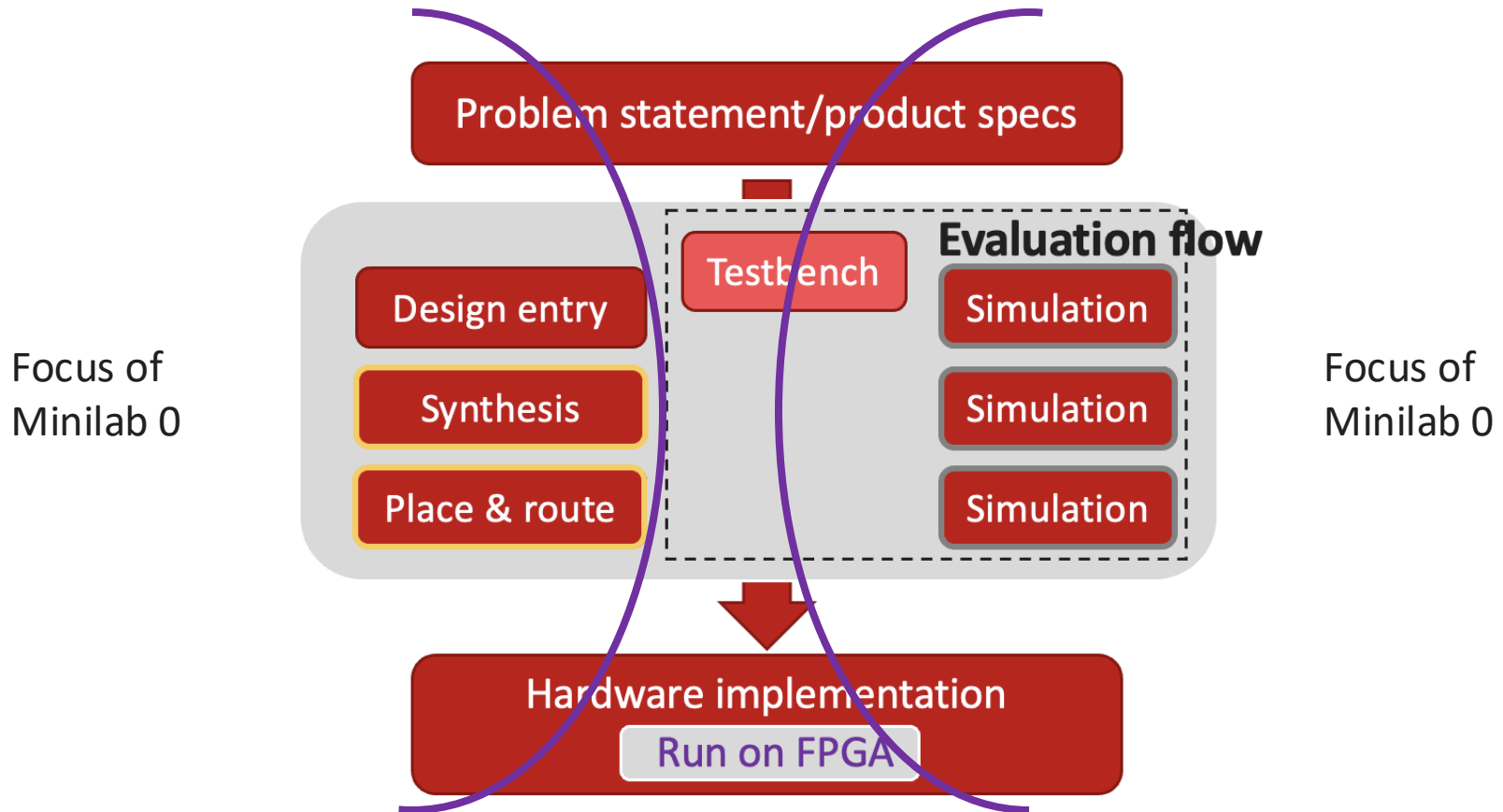



# Design validation

❑ Test and debug at several steps in the process

➤ At architecture level - functional simulation of HDL.

➤ At RTL level - functional simulation of RTL HDL.

➤ At logic design or synthesis - functional simulation of gate-level circuit.


➤ At implementation - timing simulation of schematic, netlist or HDL with implementation-based timing information (functional simulation can also be useful here).

➤ At programmed FPGA level - in-circuit test of function and timing.

Minilab 1  
Part 1

Minilab 1  
Part 2

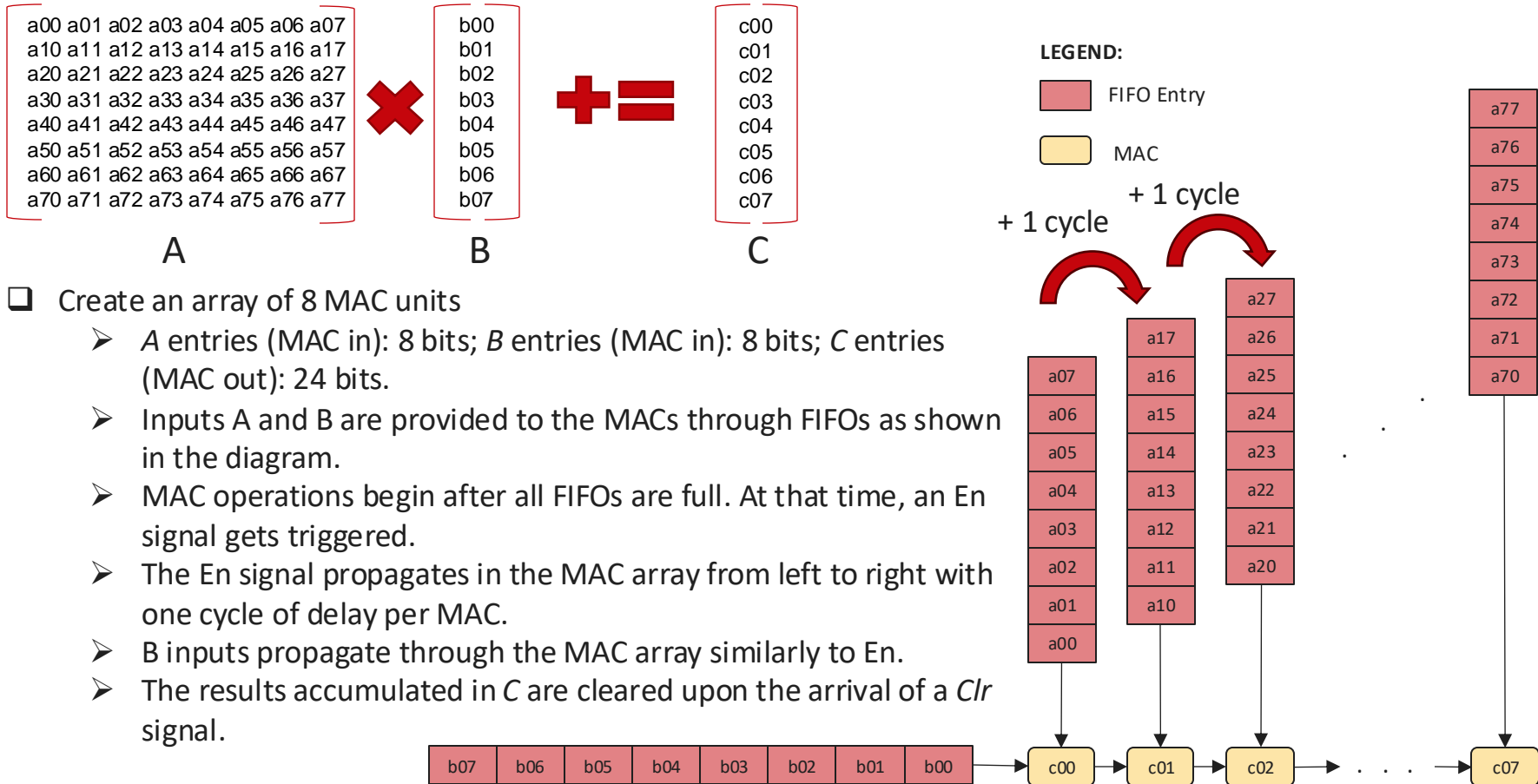
# Example design: matrix-vector multiplication



- ❑ Create an array of 8 MAC units
  - A entries (MAC in): 8 bits; B entries (MAC in): 8 bits; C entries (MAC out): 24 bits.
  - Inputs A and B are provided to the MACs through FIFOs as shown in the diagram.
  - MAC operations begin after all FIFOs are full. At that time, an En signal gets triggered.
  - The En signal propagates in the MAC array from left to right with one cycle of delay per MAC.
  - B inputs propagate through the MAC array similarly to En.
  - The results accumulated in C are cleared upon the arrival of a Clr signal.



# Instantiating Regular Structures

 

```
module vector_reduce(input [15:0] vec [7:0],
                    output [15:0] sum);
logic [15:0] sums [8:0]; // note extra wiring
always_comb begin
    sums[0] = 0;
    for(int i=0; i<8; ++i) begin
        sums[i+1] = sums[i] + vec[i];
    end // for
end // always_comb
endmodule // vector_reduce
```

```
module vector_reduce(input [15:0] vec [7:0],
                    output [15:0] sum);
logic [15:0] sums [8:0]; // note extra wiring
assign sums[0] = 0;
assign sum = sums[8];
genvar i;
generate
    for (i=0; i < 8; ++i) begin
        myadder (.op1(vec[i]),
                .op2(sums[i]),
                .sum(sums[i+1]));
    end // for(i
endgenerate
endmodule // vector_reduce
```



# Part 1

- ❑ Part 1 consists of 2 subparts.
  - ❑ Part 1a: Complete the design and simulate it with a testbench.
    - ❑ A memory module with a **.mif** file is provided along with the required IP files. The memory module has a partial implementation of INTEL Avalon MM slave interface. Apart from the matrix-vector multiplication module, design a module that fetches data from the provided memory module to fill the FIFOs. Look at Tables 1 & 2 and Figure 7 [here](#) for more details on Avalon MM Interface.
    - ❑ The testbench should print all interface signals, states, and output signals.
    - ❑ Use this command to simulate in QuestaSim.  

```
vsim work.<your_testbench_name>_tb -L  
C:/intelFPGA_lite/21.1/questa_fse/intel/verilog/altera_mf -voptargs="+acc"
```
  - ❑ Part 1b: Fix design to meet timing constraints.
    - ❑ Change the clock in the Synopsys Design Constraint (.sdc) file to 200 MHz by changing the clock period (in nanoseconds).
    - ❑ Synthesize the design again and see if it meets timing by looking at the reports from the **Timing Analyzer**. Here is a [helpful video](#) that shows how to do it.
    - ❑ Fix the design to meet the timing requirements of the 200 MHz clock.



## Part 2

❑ Part 2 also consists of 2 subparts.

❑ Part 2a:

- Use LEDs to display and track the states of your top-level state-machine.
- Use 7-segment display the outputs of the MACs. (Please)

Note 1: Use switches to control the displays. The board has 10 switches; so, there are  $2^{10}$  different ways of control.

Note 2: Minilab 0 codes may be handy.

❑ Part 2b: Use [SignalTap](#) to ensure that you have implemented the Avalon MM interface correctly.



# Demo

- ☐ Simulation of working design
- ☐ Timing analyzer report
- ☐ On-board testing with LEDs, 7-segment display, and switches.
- ☐ On-board testing with SignalTap





# Deliverables

- ❑ Create a new public GitHub repository for your minilab submission (1 per team).
- ❑ Push all relevant files to the repository, including your codes, testbenches, and simulation logs. If for the implementation IPs are used, also add all IP-related files.

**NOTE: Simulation log with proper print statements from the testbench that explains whether a test passed or failed. If the design failed a test, it should print where and why it failed.**

- ❑ Minilab 1 report is due on 2/4 before the start of Minilab 2.
- ❑ In your report (1 per team), explain:
  - How you tested the design via simulation (screenshot of waveform).
  - How you fixed the design to meet the timing constraint.
  - How you tested the design on board using an example and snapshot of the board that shows it.
  - How you tested the design using SignalTap (screenshot of waveform around the trigger condition).
  - Explain any difficulties that you faced during the whole process and how you overcame it.



# Questions?

